

Boolean Algebra and Logic Expressions

Buboy Bernal

1 Boolean Algebra and Logic Expressions

Boolean algebra provides a mathematical framework for analyzing and simplifying digital logic circuits. It operates on binary variables (0 and 1) with three basic operations: AND (\cdot), OR ($+$), and NOT (\overline{A}).

1.1 Basic Boolean Laws

1.1.1 Commutative Laws

- **AND Form:** $A \cdot B = B \cdot A$
- **OR Form:** $A + B = B + A$

Example:

If $A = 1$ and $B = 0$:

$$1 \cdot 0 = 0 \cdot 1 = 0$$

$$1 + 0 = 0 + 1 = 1$$

1.1.2 Associative Laws

- **AND Form:** $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- **OR Form:** $A + (B + C) = (A + B) + C$

Example:

For $A = 1, B = 0, C = 1$:

$$1 \cdot (0 \cdot 1) = (1 \cdot 0) \cdot 1 = 0$$

$$1 + (0 + 1) = (1 + 0) + 1 = 1$$

1.1.3 Distributive Laws

- **AND over OR:** $A \cdot (B + C) = A \cdot B + A \cdot C$
- **OR over AND:** $A + B \cdot C = (A + B) \cdot (A + C)$

Example:

For $A = 1, B = 0, C = 1$:

$$1 \cdot (0 + 1) = 1 \cdot 0 + 1 \cdot 1 = 1$$

$$1 + 0 \cdot 1 = (1 + 0) \cdot (1 + 1) = 1$$

1.2 De Morgan's Theorems

These are fundamental for simplifying complex Boolean expressions:

- **First Theorem:** $\overline{A \cdot B} = \overline{A} + \overline{B}$
- **Second Theorem:** $\overline{A + B} = \overline{A} \cdot \overline{B}$

Example:

For $A = 1, B = 0$:

$$\overline{1 \cdot 0} = \overline{1} + \overline{0} = 0 + 1 = 1$$

$$\overline{1 + 0} = \overline{1} \cdot \overline{0} = 0 \cdot 1 = 0$$

A	B	$\overline{A \cdot B}$	$\overline{A} + \overline{B}$	Verification
0	0	1	1	✓
0	1	1	1	✓
1	0	1	1	✓
1	1	0	0	✓

3.3 Simplification of Logic Circuits

Boolean algebra helps reduce complex circuits to simpler forms with fewer gates.

Example 1: Simplification Using Identities

Simplify $Y = A \cdot B + A \cdot \overline{B}$:

$$\begin{aligned}
 Y &= A \cdot B + A \cdot \overline{B} \\
 &= A \cdot (B + \overline{B}) \quad (\text{Distributive Law}) \\
 &= A \cdot 1 \quad (\text{Complement Law}) \\
 &= A
 \end{aligned}$$

Example 2: Applying De Morgan's Theorem

Simplify $\overline{A \cdot B} + \overline{A \cdot C}$:

$$\begin{aligned}
 \overline{A \cdot B} + \overline{A \cdot C} &= \overline{A} + \overline{B} + \overline{A} + \overline{C} \\
 &= \overline{A} + \overline{B} + \overline{C}
 \end{aligned}$$

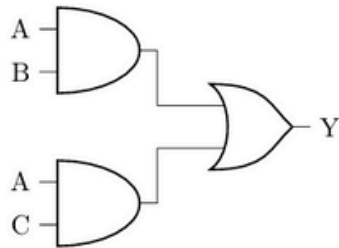


Figure 1: Original vs. Simplified Circuit

Practice Exercises

A. True or False

- F 1. () The expression $A + \overline{A}B$ simplifies to $A + B$.
F 2. () De Morgan's first theorem states $\overline{A + B} = \overline{A} \cdot \overline{B}$.
T 3. () The distributive law allows $A + BC = (A + B)(A + C)$.

B. Multiple Choice

1. Which law is used in $A(B + C) = AB + AC$?
a) Commutative b) Associative c) Distributive d) Identity
2. The simplified form of $\overline{\overline{A} + \overline{B}}$ is:
a) $A + B$ b) $A \cdot B$ c) $\overline{A} \cdot \overline{B}$ d) $\overline{A + B}$
3. If $X = \overline{A}B + A\overline{B}$, what is \overline{X} ?
a) $AB + \overline{A}\overline{B}$ b) $\overline{A}B + A\overline{B}$ c) $A + B$ d) $A \cdot B$

C. Higher-Level Thinking

1. Design Problem: Simplify $Y = \overline{A}B + \overline{A}\overline{B} + AB$ and draw the optimized circuit.
2. Proof: Using Boolean algebra, prove that $(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$.
3. Application: Explain how Boolean simplification reduces power consumption in digital circuits.

Group terms:

$$Y = \overline{A}B + \overline{A}\overline{B} + AB$$

Factor the first two terms:

$$= \overline{A}(B + \overline{B}) + AB$$

Note that $B + \overline{B} = 1$:

$$= \overline{A}(1) + AB = \overline{A} + AB$$

Now apply the Absorption Law:

$$\overline{A} + AB = \overline{A} + B$$

✅ Final simplified expression:

$$Y = \overline{A} + B$$

Optimized Circuit:

- 1 NOT gate for $A \rightarrow \overline{A}$
- 1 OR gate to combine $\overline{A} + B$

1

2

Prove:

$$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$$

Step-by-step proof:

Let's simplify the left-hand side:

Distribute $(A + B)(\overline{A} + C)$ first:

$$= (A + B)(\overline{A} + C)$$

Keep that expression.

Now multiply it with $(B + C)$:

$$= [(A + B)(\overline{A} + C)](B + C)$$

We can see that $(B + C)$ is **redundant** in this case because:

- The result of $(A + B)(\overline{A} + C)$ already **covers all 1-cases** of $(B + C)$
- So multiplying by $(B + C)$ doesn't change the outcome

✅ Therefore,

$$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$$

3

How Boolean simplification reduces power consumption:

Boolean simplification:

- **Reduces the number of logic gates** needed in a digital circuit
- **Fewer gates** means:
 - Less switching activity → **lower dynamic power**
 - Smaller chip area → **less leakage current**
 - Simpler wiring → **faster response time**
- This results in:
 - **Lower power consumption**
 - **Improved reliability**
 - **Longer battery life** in portable devices

✅ **Conclusion:** Simplifying Boolean expressions optimizes both **performance** and **power efficiency** in digital electronics.